

CS2100 - L10 - Processors : Datapath

Week
5+6


10.1 - Generic Execution Stages

10.2 - MIPS Execution Stages (FDEMW)

- [F] Fetch
- [D] Decode & Operation Fetch
- [E] Execute : ALU
- [M] Memory Access
- [W] Result Write

10.3 - Constructing Datapath

10.1 - Generic Execution Stages

 

■ **Fetch:**

- ❑ Get instruction from memory
- ❑ Address is in **P**rogram **C**ounter (PC) Register

■ **Decode:**

- ❑ Find out the operation required

■ **Operand Fetch:**

- ❑ Get operand(s) needed for operation

■ **Execute:**

- ❑ Perform the required operation

■ **Result Write (Store):**

- ❑ Store the result of the operation

10.2 - MIPS Execution Stages (FDEMW)

5-STAGE MIPS EXECUTION

- ① same duration
② same kind of operation \Rightarrow mechanism

Design changes:

- Merge *Decode* and *Operand Fetch* – Decode is simple for MIPS
- Split *Execute* into **ALU** (Calculation) and **Memory Access**

F
D
E
M
W

	add \$3, \$1, \$2	lw \$3, 20(\$1)	beq \$1, \$2, label
Fetch	Read inst. at [PC]	Read inst. at [PC]	Read inst. at [PC]
Decode & Operand Fetch	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Read [\$2] as <i>opr2</i>
ALU	$Result = opr1 + opr2$	$MemAddr = opr1 + opr2$	$Taken = (opr1 == opr2)?$ $Target = PC + Label*$
Memory Access		Use <i>MemAddr</i> to read from memory	
Result Write	Result stored in \$3	Memory data stored in \$3	if (<i>Taken</i>) $PC = Target$

[L09 - AY2021S1]

Simplest possible implementation of a subset of the core MIPS ISA:

Arithmetic and Logical operations

- add, sub, and, or, addi, andi, ori, slt

Data transfer instructions

- lw, sw

Branches

- beq, bne

Shift instructions (sll, srl) and J-type instructions (j) will not be discussed:

- Left as exercises ☺

①


Fetch Stage: Requirements

■ Instruction **Fetch Stage**:

1. Use the **Program Counter (PC)** to fetch the instruction from **memory**
 - PC is implemented as a special register in the processor
2. **Increment** the PC by 4 to get the address of the next instruction:
 - How do we know the next instruction is at PC+4?
 - Note the exception when branch/jump instruction is executed

■ Output to the next stage (**Decode**):


- The instruction to be executed

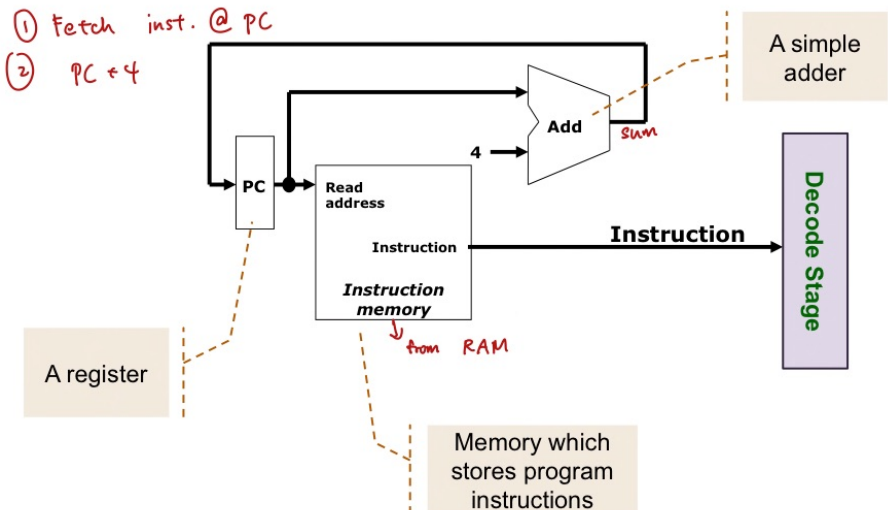

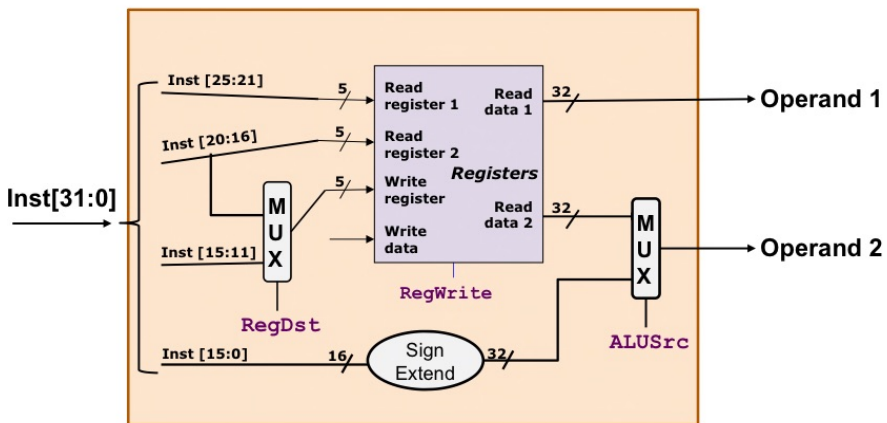(2)

Decode Stage: Requirement

- Instruction **Decode Stage**:
 - Gather data from the instruction fields:
 1. Read the **opcode** to determine instruction type and field lengths
 2. Read data from all necessary registers
 - Can be two (e.g. **add**), one (e.g. **addi**) or zero (e.g. **j**)
- Input from previous stage (**Fetch**):
 - Instruction to be executed
- Output to the next stage (**Execute**):
 - Operation and the necessary operands



③ ALU Stage: Requirement

■ Instruction **ALU Stage**:

- **ALU = Arithmetic-Logic Unit**
- Perform the real work for most instructions here
 - Arithmetic (e.g. **add**, **sub**), Shifting (e.g. **sll**), Logical (e.g. **and**, **or**)
 - Memory operation (e.g. **lw**, **sw**): Address calculation
 - Branch operation (e.g. **bne**, **beq**): Perform register comparison and target address calculation

■ Input from previous stage (**Decode**):

- Operation and Operand(s)

■ Output to the next stage (**Memory**):


- Calculation result

Categorise into :


① Non-branch instructions

② Branch instructions

[E] Non-Branch Instructions

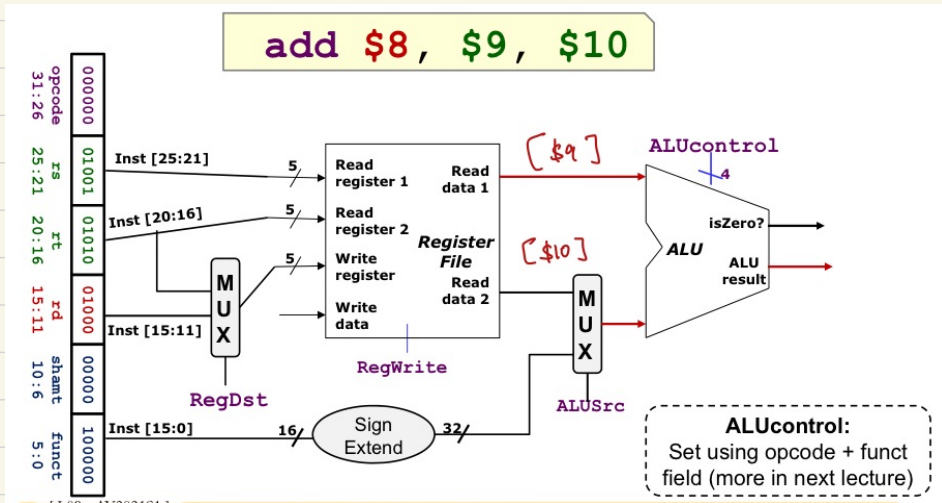

[E] Branch Instructions

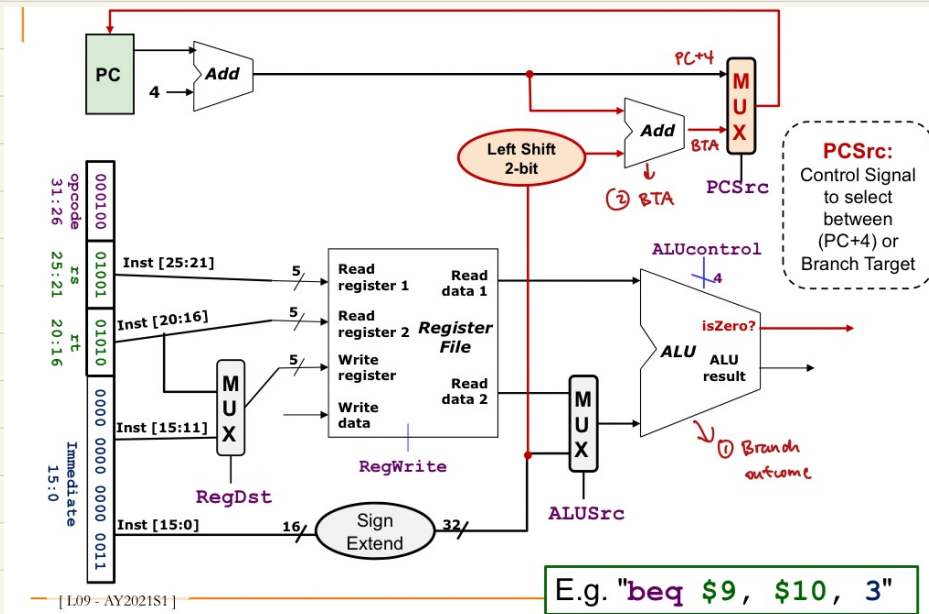

$\hookrightarrow [\$9] == [\$10] \Rightarrow [\$9] - [\$10] \text{ isZero?}$


[M] Memory Access

(4) Memory Stage: Requirement

Only for
lw/sw/
lb/sb !!!

■ Instruction **Memory Access Stage**:

- Only the load and store instructions need to perform operation in this stage:
 - Use memory address calculated by ALU Stage
 - Read from or write to data memory
- All other instructions remain idle
 - Result from ALU Stage will pass through to be used in Result Store stage if applicable
- Input from previous stage (**ALU**):
 - Computation result to be used as memory address (if applicable)
- Output to the next stage (**Result Write**):
 - Result to be stored (if applicable)

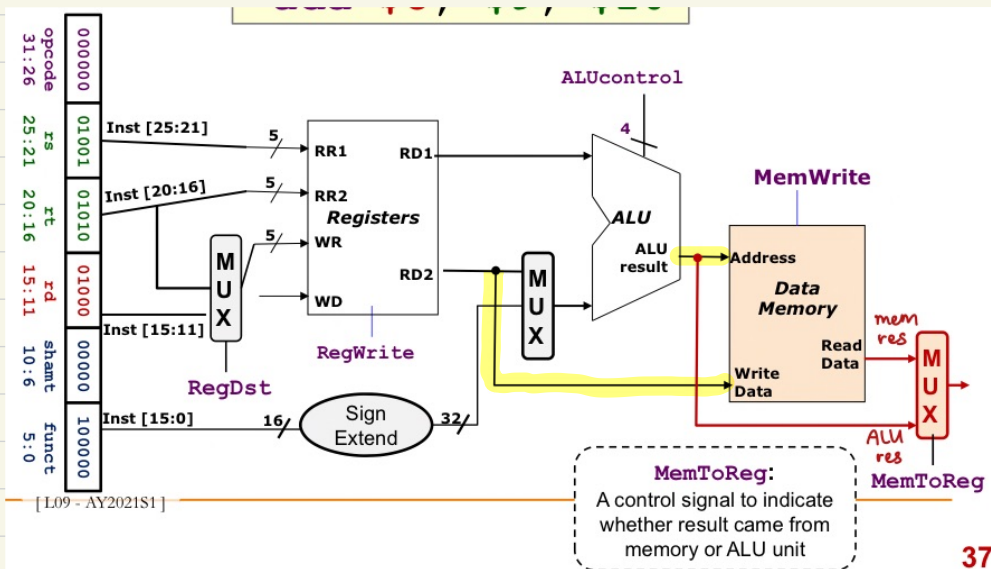

⑤


Result Write Stage: Requirement

■ Instruction **Register Write Stage**:

- Most instructions write the result of some computation into a register
 - Examples: arithmetic, logical, shifts, loads, set-less-than
 - Need destination register number and computation result
- Exceptions are stores, branches, jumps:
 - There are no result to be written
 - These instructions remain idle in this stage

■ Input from previous stage (**Memory**):

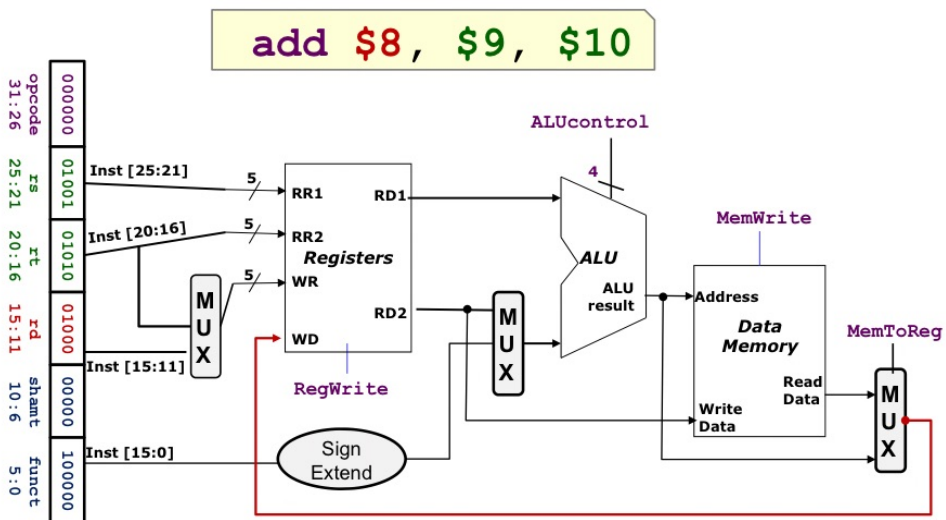- Computation result either from memory or ALU



10.3 - Constructing Datapath

Shifting and jumping are not supported!

