

# CS2100 - L21a - Sequential Logic (Building Blocks)

## 21a.1 - Memory elements

### 21a.2 - Latches

- S-R latch
- D latch


### 21a.3 - Flip-flops

- S-R flip-flop
- D flip-flop
- J-K flip-flop
- T flip-flop

## 21a.1 - Memory elements
 
### Memory Elements: Overview

- A device which can remember value indefinitely, or change value on command from its inputs.



- Characteristic table:

Diff ← from truth table

Command (at time $t$ )	<sup>now</sup> $Q(t)$	<sup>current</sup> $Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1

$Q(t)$  or  $Q$ : current state  
 $Q(t+1)$  or  $Q^+$ : next state


[ L21a - AY2021S1 ]

### Memory Elements: Triggering/Activation

- Two types of triggering/activation

#### 1. Pulse-triggered

- Latches
- ON = 1, OFF = 0

 

#### 2. Edge-triggered

- Flip-flops
- Positive edge-triggered (ON = from 0 to 1; OFF = other time)
- Negative edge-triggered (ON = from 1 to 0; OFF = other time)


[ L20a - AY1920S1 ]

## 21a.2 - Latches

### S-R latch
 
#### **S-R Latch:** Overview

- **Two inputs:** [ **S** and **R** ]
- **Two complementary outputs:** [ **Q** and **Q'** ]
  - When **Q = HIGH** → latch is in **SET** state
  - When **Q = LOW** → latch is in **RESET** state



- **Two variants:**


- **Active high input S-R Latch** (1 = active)
- **Active low input S-R Latch** (0 = active)

[ L21a - AY2021S1 ]

#### **Active High S-R Latch: Characteristic**

- **Characteristic table:**

S	R	Q	Q'	Action
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

 



S	R	Q(t+1)	or Q <sup>+</sup>
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	indeterminate	

$$\left\{ \begin{array}{l} Q(t+1) = ? \quad S + R' \cdot Q \\ S \cdot R = 0 \end{array} \right.$$

[ L21a - AY2021S1 ]
  
## Active-Low $S$ - $R$ Latch

- **Active-low input**  $S$ - $R$  latches are similarly constructed with cross-coupled NAND gates:





(Sometimes, the inputs are labelled as  $S'$  and  $R'$ .)

- Note the alternative drawing on the right, where NAND gate is drawn as Negative-OR gate
- In this case,
  - when  $R=0$  and  $S=1$ , the latch is **reset** (i.e.  $Q$  becomes 0)
  - when  $R=1$  and  $S=0$ , the latch is **set** (i.e.  $Q$  becomes 1)
  - when  $S=R=1$ , it is a **no-change** command.
  - when  $S=R=0$ , it is an **invalid** command.

[L21a - AY2021S1]
  
## Gated $S$ - $R$ Latch (with enable)

- $S$ - $R$  latch + *enable input* ( $EN$ ) and 2 AND gates  $\rightarrow$  a **gated  $S$ - $R$  latch**



- Outputs change (if necessary) only when  **$EN$  is high**

[L21a - AY2021S1]


## D latch

### Gated **D** Latch: Overview

*direct/data*

- Make input  $R$  equal to  $S'$  → **gated D latch**

*Give only one input*

 

- D latch eliminates the **undesirable condition of invalid state in the S-R latch**

[ L21a - AY2021S1 ]

### Gated **D** Latch: Characteristic

- When  $EN$  is high,
  - $D = \text{HIGH} \rightarrow$  latch is SET
  - $D = \text{LOW} \rightarrow$  latch is RESET
- Hence when  $EN$  is high,  $Q$  “follows” the  $D$  (data) input.
- **Characteristic table:**

$EN$	$D$	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change


When  $EN=1$ ,  $Q(t+1) = ? \mathcal{D}$

[ L21a - AY2021S1 ]

## 21a.3 - Flip-flops
 
### Flip-Flops: Variants

- **S-R flip-flop**, **D flip-flop**, **J-K flip-flop** and **T flip-flop**
- Note the ">" symbol at the clock input.




[ L21a - AY2021S1 ]

## S-R flip-flop
 
### S-R Flip-Flop

- **On the triggering edge of the clock pulse,**
  - $R = \text{HIGH}$  and  $S = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
  - $S = \text{HIGH}$  and  $R = \text{LOW} \rightarrow Q$  becomes HIGH (SET state)
  - Both  $R$  and  $S$  are LOW  $\rightarrow$  No change in output  $Q$
  - Both  $R$  and  $S$  are HIGH  $\rightarrow$  Invalid!
- **Characteristic table** of positive edge-triggered S-R flip-flop:



S	R	CLK	Q(t+1)	Comments
0	0	X	Q(t)	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	?	Invalid

X = irrelevant ("don't care")


↑ = clock transition LOW to HIGH

[ L21a - AY2021S1 ]

## D flip-flop
 
### D Flip-Flop: Summary

- Single input  $D$  (data), on the triggering edge of the clock pulse:
  - $D = \text{HIGH} \rightarrow Q$  becomes HIGH (SET state)
  - $D = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
- Hence,  $Q$  “follows”  $D$  at the clock edge.
- Convert  $S$ - $R$  flip-flop into a  $D$  flip-flop: **add an inverter**



$D$	$CLK$	$Q(t+1)$	Comments
1	$\uparrow$	1	Set
0	$\uparrow$	0	Reset


$\uparrow$  = clock transition LOW to HIGH

[ L21a - AY2021S1 ]

## J-K flip-flop
 
### J-K Flip-Flop

- $Q$  and  $Q'$  are fed back to the pulse-steering NAND gates



- Characteristic table:**

$J$	$K$	$CLK$	$Q(t+1)$	Comments
0	0	$\uparrow$	$Q(t)$	No change
0	1	$\uparrow$	0	Reset
1	0	$\uparrow$	1	Set
1	1	$\uparrow$	$Q(t)'$	Toggle

$Q(t+1) = ?$

No illegal state!


[ L21a - AY2021S1 ]

## T Flip-flop
 
### T Flip-Flop

*toggle*

- Formed by tying both inputs of J-K Flip-Flop together:



- Characteristic table:**

T	CLK	$Q(t+1)$	Comments
0	↑	$Q(t)$	No change
1	↑	$Q(t)'$	Toggle

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = ?$$

[L21a - AY2021S1]

## Flip-Flop Characteristic Tables

- Summary of the 4 flip-flops covered:

J	K	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

S	R	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

D	$Q(t+1)$
0	0 Reset
1	1 Set

T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q(t)'$ Toggle

[L21b - AY2021S1]