

# CS2100 - L19 - Combinational Circuits

## 19.1 - Design methods

## 19.2 - Gate-level design

- Half-adder
- Full-adder

## 19.3 - Block-level design

- Parallel adders
- Adder cum subtractor

## 19.4 - Arithmetic circuits

- Magnitude comparator

## 19.5 - Circuit delays

## Design Methods

- Different combinational circuit design methods:
  - a. Gate-level design method (with logic gates)
  - b. Block-level design method (with functional blocks)
- Design methods make use of logic gates and useful function blocks
  - ❑ These are available as Integrated Circuit (IC) chips
  - ❑ Types of IC chips (based on packing density): SSI, MSI, LSI, VLSI, ULSI
- Main objectives of circuit design:
  - ❑ Reduce cost (number of gates for small circuits; number of IC packages for complex circuits)
  - ❑ Increase speed
  - ❑ Design simplicity (re-use blocks where possible)

## 19.2 - Gate-level design

### Half-adder

#### Gate-Level (SSI) Design: **Half Adder** (1/2)


##### ■ Design procedure:

###### 1. State problem

Example: Build a **Half Adder**

###### 2. Determine and label the inputs and outputs of circuit

 Example: Two inputs and two outputs labeled, as shown below



X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

###### 3. Draw the truth table

#### Gate-Level (SSI) Design: **Half Adder** (2/2)

##### 4. Obtain simplified Boolean functions


Example:  $C = X \cdot Y$

$S = X' \cdot Y + X \cdot Y'$


S can be further simplified to  $X \oplus Y$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

##### 5. Draw logic diagram:

 

**Half Adder**

 


## Full-adder

### Gate-Level (SSI) Design: **Full Adder**(1/5)

- Half adder adds up only two bits
- Addition of two binary numbers need to add 3 bits
  - including the **carry** →

	1	1	1	Carry
	0	0	1	1
+	0	1	1	1
	1	0	1	0
				S

 - Need a **Full Adder** (so called as it can be made from two half adders)



### Gate-Level (SSI) Design: **Full Adder**(2/5)

- Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

- Z - carry in (to the current position)
- C - carry out (to the next position)

- Using K-map, simplified SOP form:

**C =**


YZ \ X	00	01	11	10
0			1	
1		1	1	1

**S =**

YZ \ X	00	01	11	10
0		1		1
1	1		1	
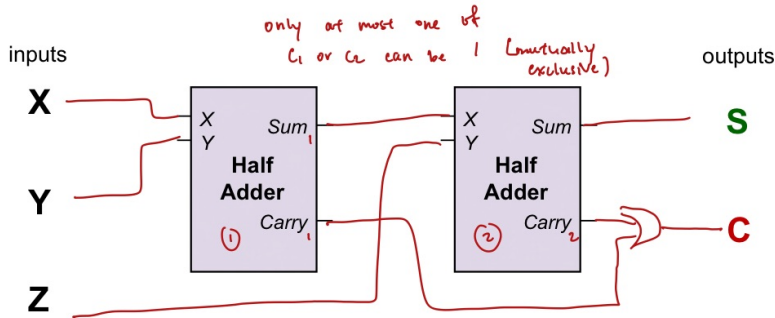
## Gate-Level (SSI) Design: **Full Adder**(3/5)

- Alternatively, can you construct the full-adder using **two half adders** and a suitable logic gate?




- This is an example of **block level design**

## Gate-Level (SSI) Design: **Full Adder**(4/5)

- If we trace the internal circuit, we get:

$$C = X \cdot Y + (X \oplus Y) \cdot Z$$
 
$$S = X \oplus (Y \oplus Z) = (X \oplus Y) \oplus Z \text{ (XOR is associative)}$$



## Block-Level Design



- More complex circuits can also be built using block-level method
- General idea for block-level design method:
  - Decomposing the main problem to sub-problems recursively
  - Until sub-problem is small enough to be directly solved by blocks of circuits
- Simple examples using 4-bit parallel adder as building blocks:
  1. **16-bit Parallel Adder**
  2. **Adder cum Subtractor**

## Parallel adders

### Revision: Parallel Adder


- 4-bit parallel adder

$C_5$	$C_4$	$C_3$	$C_2$	$C_1$	Carry
$X_4$	$X_3$	$X_2$	$X_1$	$X$	
$+$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y$
					$S$
$S_4$	$S_3$	$S_2$	$S_1$		

  

 
## 16-Bit Parallel Adder

- Larger parallel adders can be built from smaller ones
- Example: A 16-bit parallel adder can be constructed from four 4-bit parallel adders:



A 16-bit parallel adder

 

## 4-Bit Adder Cum Subtractor: **Key Idea**

■ Recall:


$$\begin{aligned}
 X - Y &= X + (-Y) \\
 &= X + (2s \text{ complement of } Y) \\
 &= X + (1s \text{ complement of } Y) + 1
 \end{aligned}$$

↓  
flip all bits

■ Think:

- How do we use **Block Level Design** using **4-bit Parallel Adder** and **suitable logic gate(s)** to implement such a circuit?
 
## EX: 4-Bit Adder Cum Subtractor: **Circuit**





## 19.4 - Arithmetic circuits

### Magnitude comparator

#### Magnitude Comparator: **Insight**


$A_4$	$A_3$	$A_2$	$A_1$	$A$	$1$	$1$	$0$	$0$	$A$	$0$	$0$	$1$	$1$	$A$
compare with					compare with					compare with				
$B_4$	$B_3$	$B_2$	$B_1$	$B$	$0$	$1$	$0$	$1$	$B$	$0$	$1$	$1$	$0$	$B$
					<b>A Larger!</b>					<b>B Larger!</b>				

#### ■ Formulate the observation:

- If  $((A_4.B_4')$  or  $(A_4 == B_4).(A_3.B_3')$  or .....):
  - A is larger
- Else if  $((A_4'.B_4)$  or  $(A_4 == B_4).(A_3'.B_3)$  or .....):
  - B is larger
- Else if  $((A_4 == B_4)$  and  $(A_3 == B_3)$  .....):
  - A and B are the same!
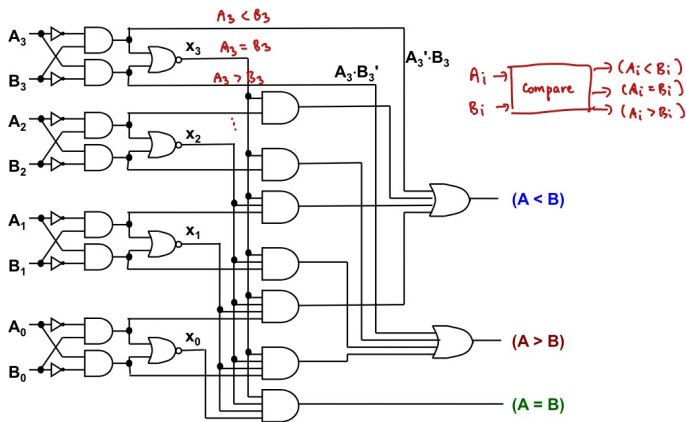
#### Magnitude Comparator: **Circuit**


Let  $A = A_3A_2A_1A_0$      $B = B_3B_2B_1B_0$      $x_i = A_i \cdot B_i + A_i' \cdot B_i'$



## 19.5 - Circuit delays

 
### Circuit Delays: Definition & Formula

- Given a logic gate with delay  $t$ . If inputs are stable at times  $t_1, t_2, \dots, t_n$ , then the earliest time in which the output will be stable is:



- Repeat above rule for all gates to calculate the delays of all outputs of a combinational circuit

### Circuit Delays: More Complex Example

 

- How about 4-bit parallel adder ?
  - The last signal to be generated is C<sub>5</sub> at time 9t