

17.1 - Logic gates

17.2 - Universal gates

17.3 - Standard forms



- Terminology
- SOP and POS

17.4 - Minterms & maxterms

- Sum of minterms
- Product of maxterms


Inverter / AND / OR Gates

Inverter (NOT gate)

  


| A | A' |
|---|----|
| 0 | 1 |
| 1 | 0 |

AND gate

 

| A | B | A · B |
|---|---|-------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |


OR gate

 

| A | B | A + B |
|---|---|-------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |


NAND/NOR Gates

NAND gate

 

| A | B | $(A \cdot B)'$ |
|---|---|----------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

NOR gate

 


| A | B | $(A + B)'$ |
|---|---|------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

[L17 - AY2021S1]


XOR/XNOR Gates

XOR gate

 

| A | B | $A \oplus B$ |
|---|---|--------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

XNOR gate

 

XNOR can be represented by \odot (Example: $A \odot B$)


| A | B | $(A \oplus B)'$ |
|---|---|-----------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

[L17 - AY2021S1]

17.2 - Universal gates

- **Fan-in**: the number of inputs of a gate
- Gates may have fan-in more than 2

□ Example: a **3-input AND gate**

 

Universal Gates

- { **NOT**, **AND**, **OR** } gates are sufficient for building any Boolean function
 - Also known as **set of universal gates**
- There are other sets of universal gate:
 - { **NAND** } (i.e. 1 gate is suffice)
 - { **NOR** }


{ **NAND** } is a **Universal Gate**

■ **Proof:**


Implement **NOT** / **AND** / **OR** using only **NAND** gates


 
$$(x \cdot x)' = x' \quad (\text{idempotency})$$


 
$$\begin{aligned} ((x \cdot y)' \cdot (x \cdot y)')' &= ((x \cdot y)')' & (\text{idempotency}) \\ &= x \cdot y & (\text{involution}) \end{aligned}$$




$$\begin{aligned} ((x \cdot x)' \cdot (y \cdot y)')' &= (x' \cdot y')' & (\text{idempotency}) \\ &= (x')' + (y')' & (\text{DeMorgan}) \\ &= x + y & (\text{involution}) \end{aligned}$$

[L17 - AY2021S1]

*idea: duality: **NOR** and **NAND** gate are dual forms of each other!?*
*todo: do this direct mirror image of the **NAND** gate*

EX: **NOR** Gate

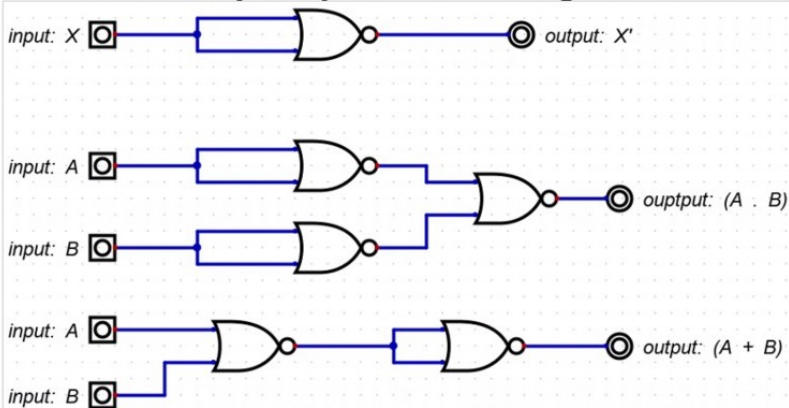■ Show that {**NOR**} is a universal gate



17.3 - Standard forms

Standard Forms

- Types of Boolean expressions that lead to simple circuit translation
- **Terminology:**

Literals

- A Boolean variable on its own or in its complemented form
- Examples: x , x' , y , y'

Product term

- A single literal or a logical product (AND) of several literals
- Examples: x , $x \cdot y \cdot z'$, $A' \cdot B$, $A \cdot B$, $d \cdot g' \cdot v \cdot w$

Sum term

- A single literal or a logical sum (OR) of several literals
- Examples: x , $x + y + z'$, $A' + B$, $A + B$, $c + d + h' + j$

[L17 - AY2021S1]

SOP and POS Standard Forms

Sum-of-Products (SOP)

- A product term or a logical sum (OR) of several product terms
- Examples: x , $x + y \cdot z'$, $x \cdot y' + x' \cdot y \cdot z$, $A \cdot B + A' \cdot B'$, $A + B' \cdot C + A \cdot C' + C \cdot D$

Product-of-Sums (POS)

- A sum term or a logical product (AND) of several sum terms
- Examples: x , $x \cdot (y + z')$, $(A + B) \cdot (A' + B')$, $(A + B + C) \cdot D' \cdot (B' + D + E')$

- All Boolean expression can be expressed in **SOP** or **POS**

[L17 - AY2021S1]

SOP → 2-Level AND-OR Circuit

- An **SOP** expression can be easily implemented using

1. 2-level AND-OR circuit
2. 2-level NAND circuit

1st level: construct each product term
2nd level: pluck all into OR gate

POS → 2-Level OR-AND Circuit



- A POS expression can be easily implemented using

1. 2-level OR-AND circuit
2. 2-level NOR circuit

1st level: construct each sum term
2nd level: pluck all into AND gate

Mirror
image
of SOP

Canonical Forms

- Canonical / normal form: a **unique form** of representation

↗ Specialized form of SOP

1. **Sum-of-minterms** = Canonical sum-of-products

2. **Product-of-maxterms** = Canonical product-of-sums
↓ Specialized form of POS

Minterm & Maxterm: Definition

Minterm

- A **minterm** of n variables is a product term that contains n **literals** from all the variables.
- Example: On 2 variables x and y , the minterms are: $x' \cdot y'$, $x' \cdot y$, $x \cdot y'$ and $x \cdot y$

Maxterm

- A **maxterm** of n variables is a sum term that contains n **literals** from all the variables.
- Example: On 2 variables x and y , the maxterms are: $x' + y'$, $x' + y$, $x + y'$ and $x + y$

- In general, with n variables we have 2^n minterms and 2^n maxterms

Minterm & Maxterm: Terminology

| x | y | Minterms | | Maxterms | |
|---|---|---------------|-----------|----------|-----------|
| | | Term | Notation | Term | Notation |
| 0 | 0 | $x' \cdot y'$ | m0 | $x+y$ | M0 |
| 0 | 1 | $x' \cdot y$ | m1 | $x+y'$ | M1 |
| 1 | 0 | $x \cdot y'$ | m2 | $x'+y$ | M2 |
| 1 | 1 | $x \cdot y$ | m3 | $x'+y'$ | M3 |

- Each minterm is the complement of the corresponding maxterm

□ E.g.: $m2 = x \cdot y'$

$$m2' = (x \cdot y')' = x' + (y')' = x' + y = M2$$

[L17 - AY2021S1]

Conversion

- $F2 = \Sigma m(1, 4, 5, 6, 7)$
 $= \Pi M(0, 2, 3)$
 (Why? How?)

| x | y | z | F2 |
|---|---|---|----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

- $F2' = m0 + m2 + m3$

- Therefore,
 $F2 = (m0 + m2 + m3)'$
 $= m0' \cdot m2' \cdot m3'$ (DeMorgan's)
 $= M0 \cdot M2 \cdot M3$ ($mx' = Mx$)

[L17 - AY2021S1]